



### ### \*\*Components and Their Details\*\*

#### 1. \*\*8254 Programmable Interval Timer (U2)\*\*

##### - \*\*Pins:\*\*

- `CLK0, CLK1, CLK2`: Clock inputs for the three timers.
- `OUT0, OUT1, OUT2`: Outputs of the three timers.
- `G0, G1, G2`: Gate inputs for enabling/disabling timers.
- `D0–D7`: Data bus for communication with the microprocessor.
- `CS`, `RD`, `WR`, `A0`, `A1`: Control signals for accessing internal registers.

##### - \*\*Purpose:\*\*

- Used to generate precise time delays and pulse widths for controlling the speed of the motor.
- Timer outputs (OUT0, OUT1) are used for motor control signals.

2. **\*\*Latch IC (U1 - 74LS373)\*\***

- **\*\*Purpose:\*\***

- Stores the address inputs (A2–A15) from the microprocessor.
- Decodes addresses to enable 8254's operation.

- **\*\*Connections:\*\***

- Receives address lines from the CPU.
- Sends address information to 8254 via A0 and A1.

3. **\*\*Flip-Flop (U3A - 74ALS112)\*\***

- **\*\*Purpose:\*\***

- Handles the direction control of the motor.
- Q and Q outputs control which H-bridge transistors are activated.

- **\*\*Connections:\*\***

- Triggered by the clock signals generated by the 8254.

4. **\*\*Open-Collector Inverters (U4A–U4D - 7406)\*\***

- **\*\*Purpose:\*\***

- Buffer and amplify control signals from the 8254.
- Drive the base of the transistors in the H-bridge.

- **\*\*Connections:\*\***

- Inputs receive signals from the flip-flop and timer outputs.
- Outputs are connected to the H-bridge transistors.

5. **\*\*H-Bridge (Transistors Q1, Q2, Q3, Q4)\*\***

- **\*\*Purpose:\*\***

- Drives the DC motor.
- Controls both the speed (via PWM signals) and direction (via flip-flop outputs).
- **Connections:**
  - The bases of the transistors are driven by the inverters (U4A–U4D).
  - The motor is connected between the diagonal pairs of transistors.

## 6. **DC Motor**

- **Purpose:**
  - Converts electrical energy into mechanical motion.
- **Connections:**
  - Connected to the H-bridge output.

## 7. **Clock Signal**

- **Purpose:**
  - Provides a consistent frequency (8 MHz) for 8254's internal operations.

## ### **How the Circuit Works**

### #### **1. Speed Control**

- **PWM Generation:**
  - The 8254 is configured to operate in a mode (e.g., Mode 2 or Mode 3) that generates Pulse Width Modulated (PWM) signals at its `OUT0` or `OUT1` outputs.
  - The duty cycle of the PWM determines the average voltage applied to the motor, which controls its speed.

- The microprocessor programs the 8254 with appropriate values to adjust the timer's reload value, thus changing the PWM frequency or duty cycle.

- **Connection:**

- `OUT0` and `OUT1` signals from the 8254 are routed through the inverters (U4A, U4B) and fed into the H-bridge transistors.

- The varying duty cycle controls the motor speed proportionally.

---

#### #### **\*\*2. Direction Control\*\***

- **Flip-Flop Operation:**

- The flip-flop (U3A) receives control signals from the microprocessor via the 8254 and toggles its outputs (`Q` and `Q'`) based on the clock input.

- The outputs of the flip-flop determine which diagonal pair of transistors in the H-bridge is activated.

- This setup reverses the polarity of the voltage applied to the motor, thus changing its direction.

- **Connection:**

- `Q` and `Q'` outputs of the flip-flop are fed into the inverters (U4C, U4D), which drive the H-bridge transistors.

---

#### ### **\*\*Sequence of Operations\*\***

1. **Initialization:**

- The microprocessor configures the 8254 via its data and control signals (`CS`, `RD`, `WR`, `A0`, `A1`).
- PWM parameters (frequency and duty cycle) are loaded into the timer registers.

## 2. **\*\*Speed Adjustment\*\***:

- The 8254 generates a PWM signal at `OUT0` or `OUT1`.
- The duty cycle of this PWM signal determines the speed of the motor.

## 3. **\*\*Direction Control\*\***:

- The flip-flop (U3A) toggles its outputs based on the control signal from the microprocessor.
- Depending on the state of `Q` and `Q`, the H-bridge changes the direction of the current through the motor, controlling its rotation direction.

## 4. **\*\*Motor Operation\*\***:

- The H-bridge transistors apply the required voltage and polarity to the motor terminals.
- The motor operates at the desired speed and direction.